
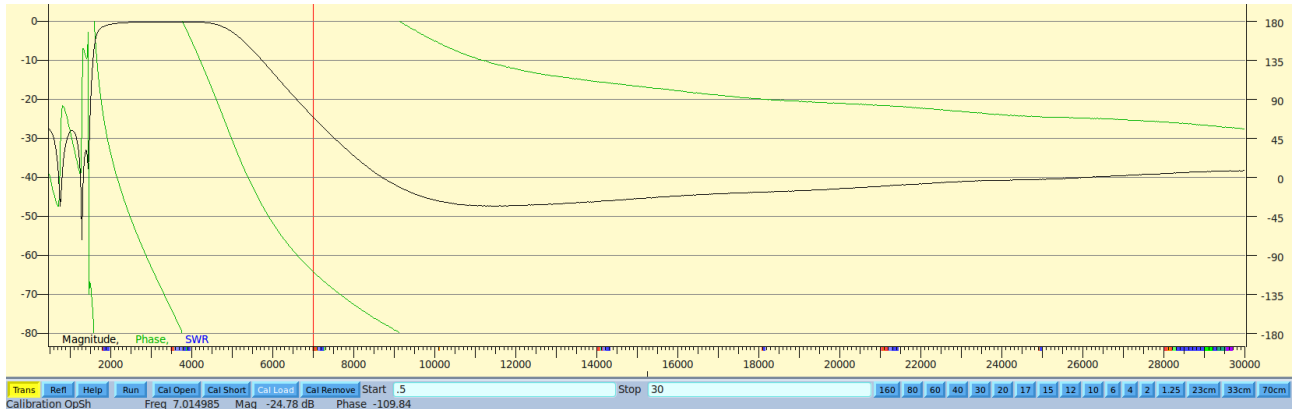


The following plots are of a 1.7 MHz HP filter cascaded with Low Pass Filters from QRP-Labs. These filters are plugged into the kitset mother board which contains the switching relays etc. Hans Summers has documented the performance of the individual filters and evaluated the toroids used <https://qrp-labs.com/images/lpkit/toroid.pdf> so a good idea of how the response is affected by cascading can be seen. The HP Filter is mounted on a single PCB on the underside of a horizontal partition in a metal case and the LP Filter is mounted on the upper side of the partition.

Plot 1.

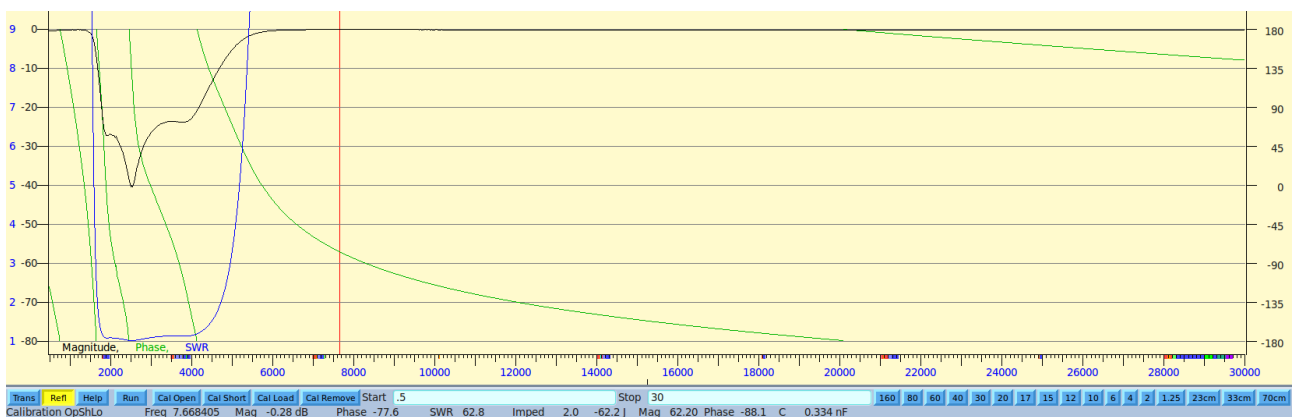

1.7 MHz HP Filter cascaded with a 4 MHz Low Pass filter in transmission mode




1.7 MHz HP Filter cascaded with a 4 MHz Low Pass filter in reflection mode

Plot 2.



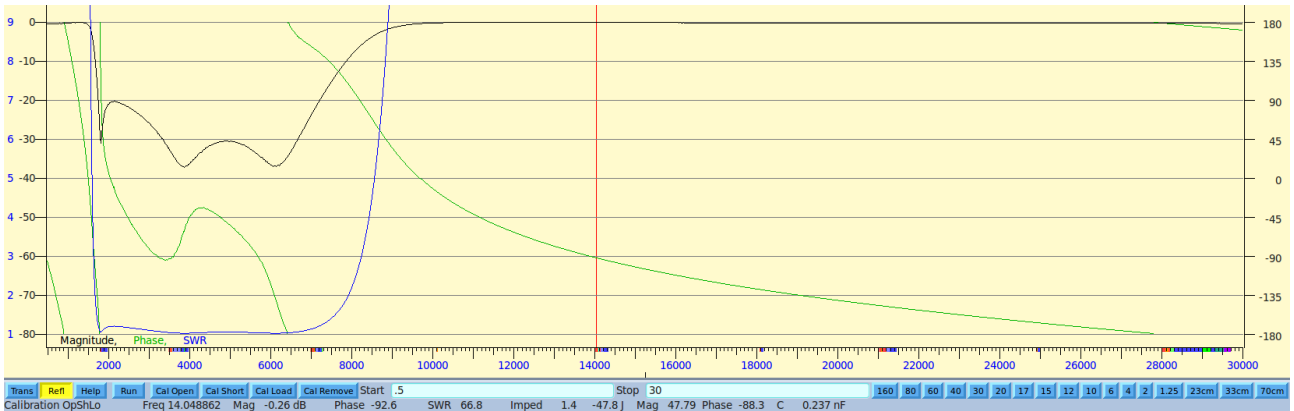1.7 MHz HP Filter cascaded with a 7 MHz Low Pass filter in transmission mode




1.7 MHz HP Filter cascaded with a 7 MHz Low Pass filter in reflection mode

Plot 3.



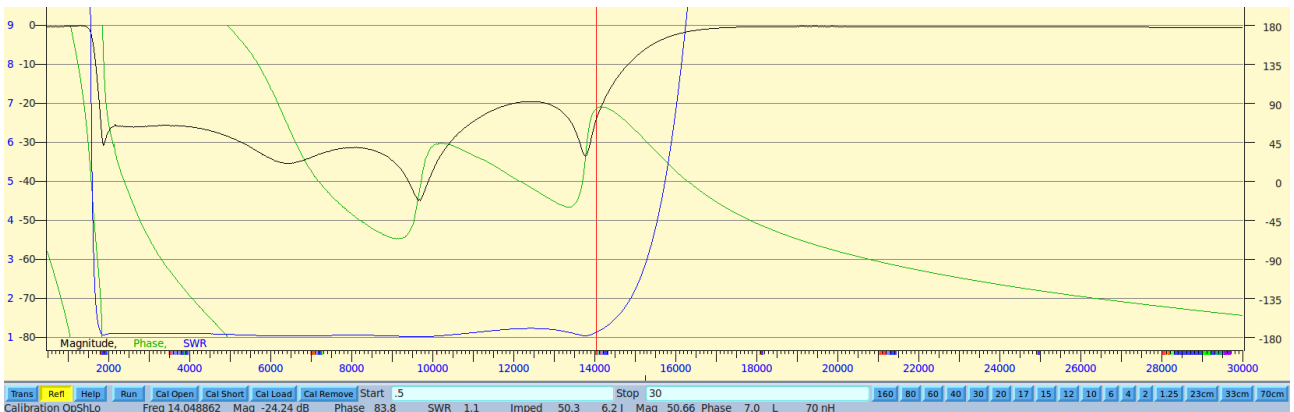1.7 MHz HP Filter cascaded with a 14 MHz Low Pass filter in transmission mode



1.7 MHz HP Filter cascaded with a 44 MHz Low Pass filter in reflection mode