

If the valve relay is open, then the polarity relay will turn the motor in closing direction, until the "close" end switch opens the circuit.

If the valve relay is closed, then the polarity relay will reverse + and - on the motor.  
The motor will turn in valve opening direction, until the "open" end switch interrupts the circuit.

gnd = Ground = 24V negative pole

